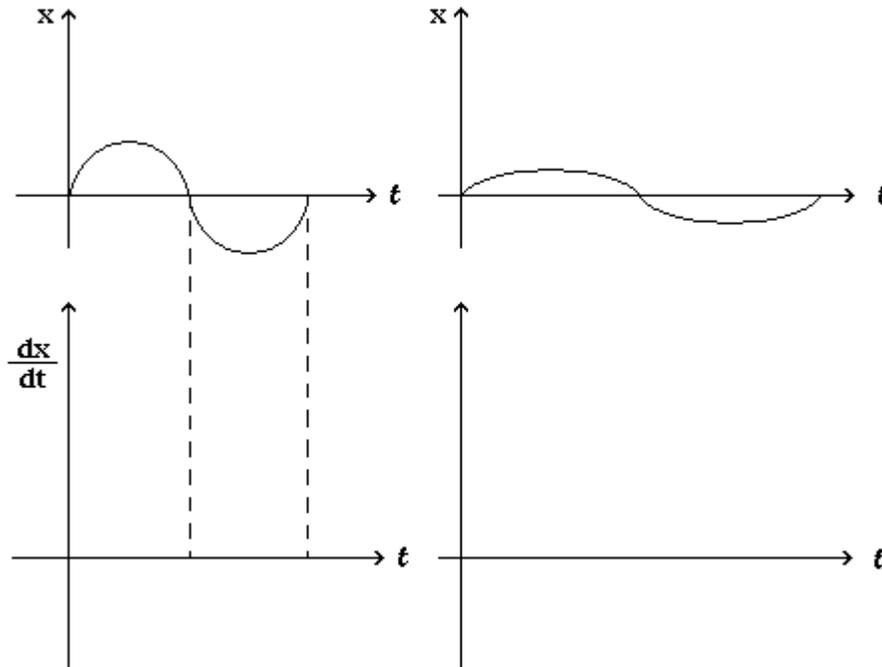


## Enhanced Guided Notes: Set 12

### Topics:

- A. Response of Basic R, L, and C Elements to a Sinusoidal Voltage/Current
- B. Frequency Response
- C. Average Power and Power Factor
- D. Rectangular/Polar Form
- E. Phasors

### A. Response of Basic R, L, and C Elements to a Sinusoidal Voltage/Current




For sinusoidal voltage

$$v(t) = V_m \sin(\omega t \pm \phi)$$

$$\frac{dv(t)}{dt} =$$

=


Resistor

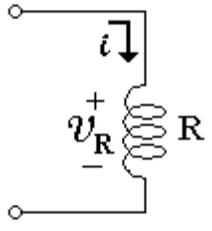

For a given  $V = V_m \sin \omega t$

$$\therefore i = V/R =$$

Where  $I_m =$   
\_\_\_\_\_

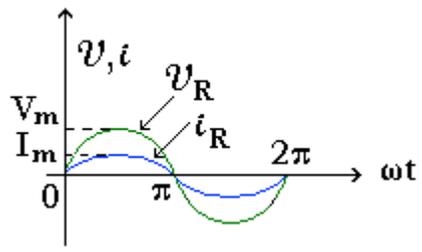

For a given  $i = I_m \sin \omega t$


$$\therefore V = iR =$$

=

Where  $V_m =$

Conclusions:


## Inductor

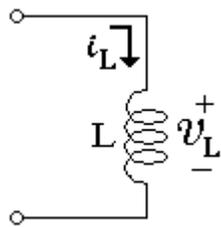

Remember  $v_L = L \frac{di_L}{dt}$

If  $i_L = I_m \sin \omega t$

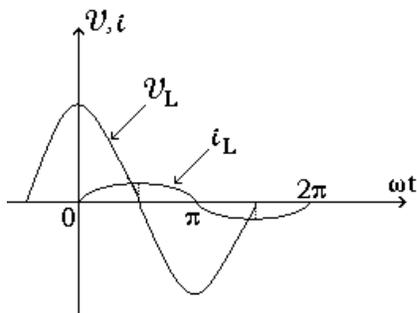Then  $v_L = L \frac{di_L}{dt} = L \omega I_m \cos \omega t$



$$v_L = L \omega I_m \cos \omega t$$

or

$$v_L = I_m X_L \cos \omega t$$

Now, what if we know  $v_L$

Remember  $i_L = \frac{1}{L} \int v_L dt$


Note,  $\omega L = \text{Reactance } (X_L)$

$$\therefore X_L = \omega L$$

$$X_L = V_m / I_m$$

Conclusions:


Capacitor

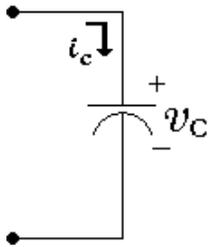

Remember,  $i_C = C \frac{dv_C}{dt}$

If  $v_C = i_m \sin \omega t$

Then  $i_C = C \frac{dv_C}{dt}$

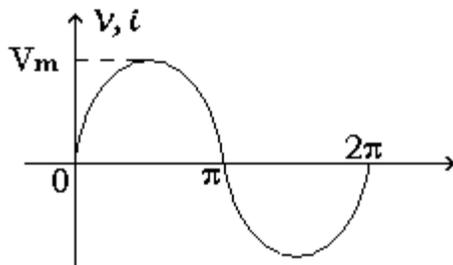

$i_C =$

$=$

If we know  $i_C \sim v_C = \int i_C dt$

Note,  $1/\omega C = \text{reactance } (X_C)$

$$\therefore X_C = 1 / \omega C$$


$$X_C = V_m / I_m$$

Conclusions:

★ The current through a 0.1 H coil is  $i = 7 \sin (377 t - 70^\circ)$

Find the sinusoidal expression for the voltage across the coil.

Sketch the  $v$  and  $i$  curves.

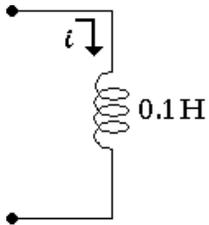

How do we approach this problem?

$$v_L =$$

Another way, use  $X_L =$

=


$$\therefore V_m =$$

=

For inductor, \_\_\_\_\_ leads \_\_\_\_\_ by \_\_\_\_\_ °

$$\therefore v_L =$$


=

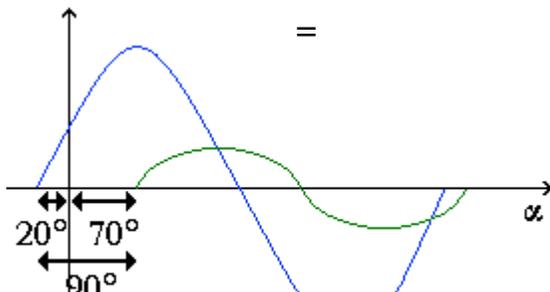

★ The current through a  $20\Omega$  inductive reactance is

$$i_L = -6 \sin(\omega t - 30^\circ)$$

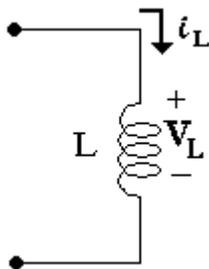What is the sinusoidal expression for the voltage?



$$i_L = -6 \sin(\omega t - 30^\circ) \sim \Rightarrow i_L =$$

$$i_L =$$

What do we need to know to solve this problem?

How do we find it?

$$\therefore \mathcal{V}_L =$$


Is there another way to solve this problem?

How?

★ The current through a  $10\ \mu$  capacitive reactance is

$$i_C = 2 \times 10^{-6} \sin(\omega t + 60^\circ)$$

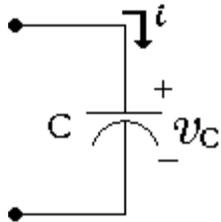Write the sinusoidal expression for the voltage.



$$i = 2 \times 10^{-6} \sin(\omega t + 60^\circ)$$

What do we need to know to solve this problem?

How do we find it?

$$\therefore V_C =$$


★ For the following pair of voltage and current, indicate whether the element involved is a capacitor, and inductor, or a resistor, and the value of C, L, or R.

$$V = 36 \sin(754t - 80^\circ)$$

$$i = 4 \sin(754t - 170^\circ)$$

How do we solve this problem?

## B. Frequency Response

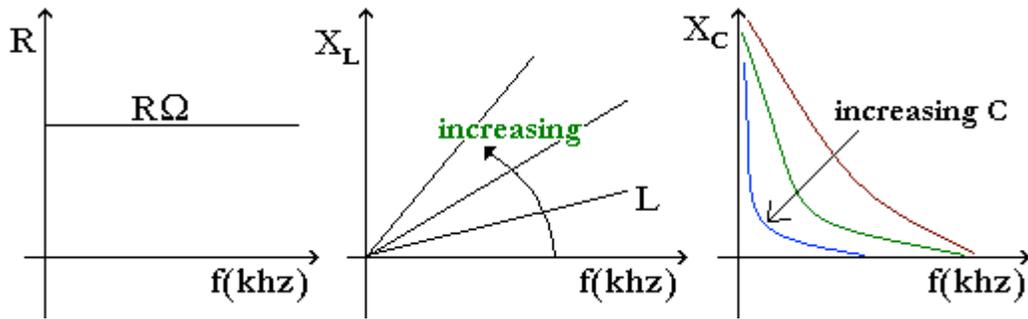

$$f = 0 \sim R = R$$

$$f \gg \sim R = R$$

$$f = 0 \sim X_L = 0$$

$$f \gg \sim X_L = \infty$$

$$f = 0 \sim X_C = \infty$$


$$f \gg \sim X_C = 0$$

Why?

★ At what frequency will the reactance of a 500 mH inductor match the resistance level of a 5kΩ resistor?
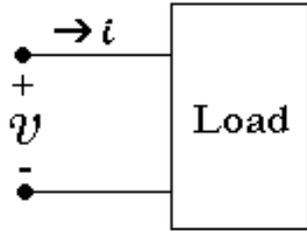
## C. Average Power and Power Factor

What will be the net transfer of power/energy? Zero?



### Resistive Load

$$P_{av} = \frac{V_m I_m}{2} = V_{Rms} I_{Rms}$$

Where  $i = I$  and  $v = V$

### Inductive/Conductance Load

$$i = I_m \sin(\omega t + \phi_i)$$

$$v = V_m \sin(\omega t + \phi_v)$$

$$P = V_m I_m \sin(\omega t + \phi_i)$$

We know that  $\sin A \sin B = \frac{\cos(A-B) - \cos(A+B)}{2}$

$$\therefore \sin(\omega t + \phi_i)$$

$$\therefore P = \frac{V_m I_m}{2} \cos \phi$$

$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P = V_{eff} I_{eff} \cos \phi$$

$$= V_{Rms} I_{Rms} \cos \phi$$

Is the magnitude of average power delivered independent of whether  $\mathcal{V}$  leads  $i$  or  $i$  leads  $\mathcal{V}$ ? Why?

Conclusions:

- In a purely resistive circuit  $\sim > P =$
- In a purely inductive circuit  $\sim > P =$
- In a purely capacitive circuit  $\sim > P =$

★ Find the average power delivered to a network having

$$i = 3 \sin (\omega t - 50^\circ)$$

$$V = 150 \sin (\omega t - 70^\circ)$$

How do we solve this problem?


Power Factor (pf) =  $\cos \phi =$  \_\_\_\_\_

Two scenarios:

◦ Resistive Load

◦ inductive/capacitive load

#### D. Rectangular / Polar Form

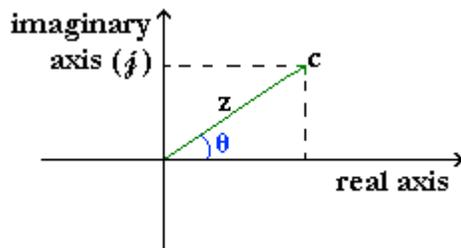

$$C = x \pm jY \quad \left. \vphantom{C} \right\} \quad z = \sqrt{x^2 + Y^2}$$


$$C = z \angle \phi \quad \phi = \tan^{-1} y/x$$

★ Convert  $C = 3 + j4$  to polar form


$$z =$$

$$\square = \tan^{-1}$$

$$\therefore C = \quad \angle$$

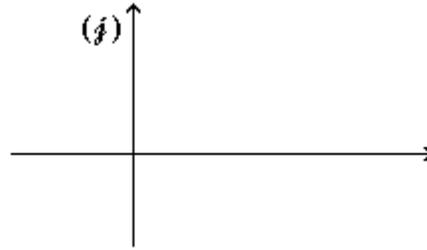

★ What if  $C = -3 + j4$

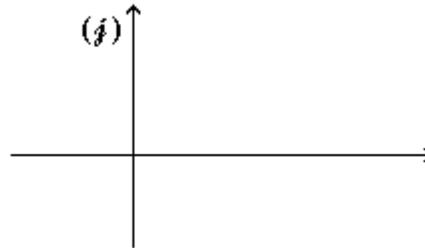


Convert  $C = 10 \angle 45^\circ$  to rectangular form

$$X =$$

$$Y =$$

$$\therefore C =$$

 

## Mathematical Operations with Complex Numbers

For  $C_1 = \pm X_1 \pm jY_1$

$C_2 = \pm X_2 \pm jY_2$

Addition  $C_1 + C_2 = (\pm X_1 \pm X_2) + j(\pm Y_1 \pm Y_2)$

Subtraction  $C_1 - C_2 = (\pm X_1 - (\pm X_2)) + j$

Multiplication  $C_1 \cdot C_2 = (X_1X_2 - Y_1Y_2) + j(Y_1X_2 + X_1Y_2)$

Division  $C_1/C_2 = \frac{X_1X_2 + Y_1Y_2}{X_2^2 + Y_2^2} + j \frac{X_2Y_1 - Y_2X_1}{X_2^2 + Y_2^2}$

**For**  $C_1 = Z_1 \angle \theta_1$

$C_2 = Z_2 \angle \theta_2$

Addition  $C_1 + C_2 = (Z_1 + Z_2) \angle \theta_1$  or  $(Z_1 + Z_2) \angle \theta_2$   
Condition?

Subtraction  $C_1 - C_2 =$   
Condition?

Multiplication  $C_1 \cdot C_2 = Z_1 Z_2 \angle \square_1 + \square_2$

Division  $C_1/C_2 = Z_1 / Z_2 \angle \square_1 + \square_2$

## E. Phasors

↓

We use RMS values instead of peak values

Time Domain

Phasor Domain

$$69.6 \sin(\omega t + 72^\circ) \quad \sim > (0.707)(69.6) \angle 72^\circ = 49.21 \angle 72^\circ$$

$$45 \cos \omega t \quad \sim >$$

★ Let  $\mathcal{V}_a = 50 \sin(377t + 30^\circ)$

$$\mathcal{V}_b = 30 \sin(377t + 60^\circ)$$

Find  $\mathcal{V}_{ab} = \mathcal{V}_a + \mathcal{V}_b$

What do we need to do now?

$$\mathcal{V}_a = \quad \rightarrow \mathbb{V}_a = \quad \angle$$

$$\mathcal{V}_b = \quad \rightarrow \mathbb{V}_b = \quad \angle$$

$$\mathbb{V}_a =$$

$$\mathbb{V}_b =$$

$$\therefore V_{ab} = V_a + V_b =$$

$$V_{ab} =$$