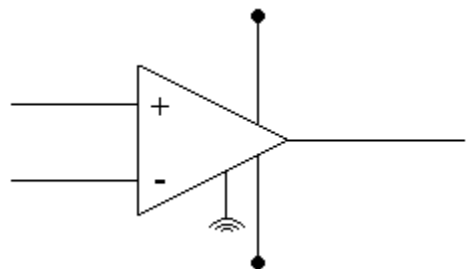


### Operational Amplifier (OP-AMP)


Operational amplifiers are devices that have very \_\_\_\_\_ input impedance and very \_\_\_\_\_ output impedance.



- ⊕ non-inverting input
- ⊖ inverting input

Output


Supply necessary to power

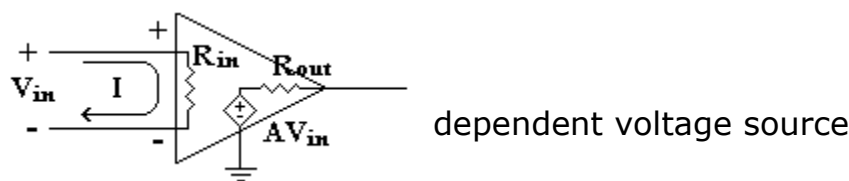

dependent voltage source

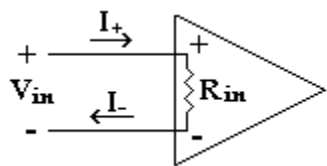
### Ideal Op-amp

Because  $R_{in}$  is very, very \_\_\_\_\_ therefore  $I$  is very, very \_\_\_\_\_



$$V+ = V-$$

$$I+ = I- = 0$$

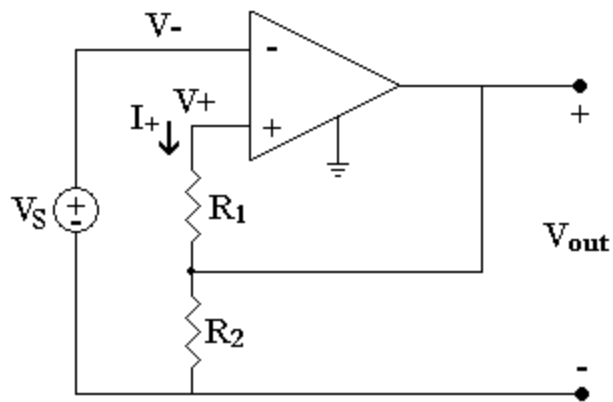

1.  $V_- = V_S$

2.  $V_+ = V_-$


3.  $I_+ = 0$

4.

5.

6.

$\therefore$

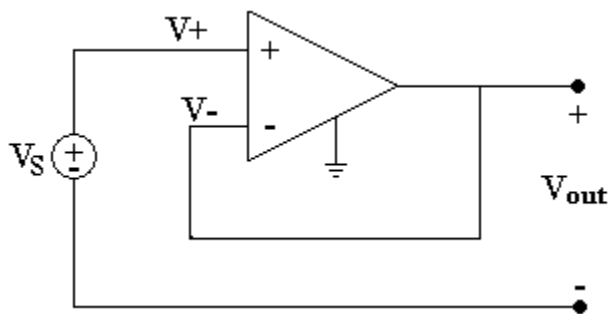


1.


2.

3.

4.

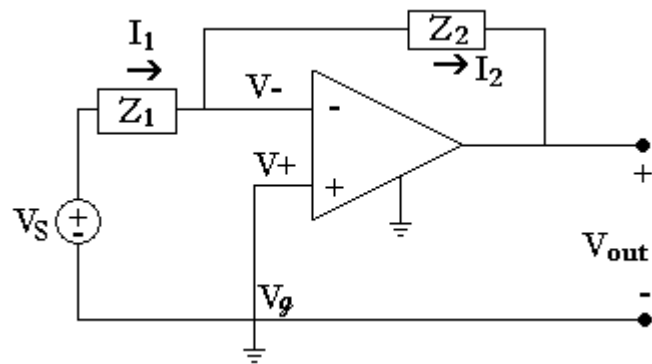

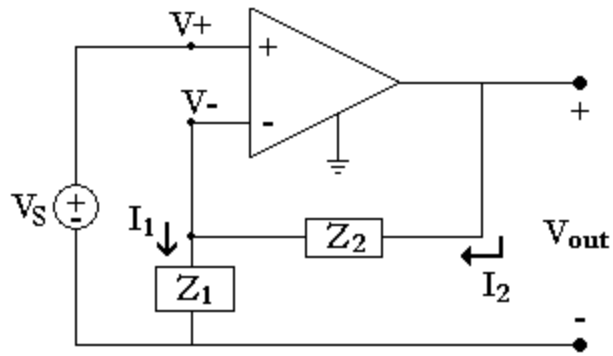1.  $V_g = 0$
2.  $V_+ = V_g = 0$
- 3.
- 4.
- 5.
- 6.
- 7.
- 8.
- $\therefore$



$$1. V_S = V_+$$

$$2. V_+ = V_-$$

$$3. V_- = V_1$$


4.

5.


6.

7.

$\therefore$

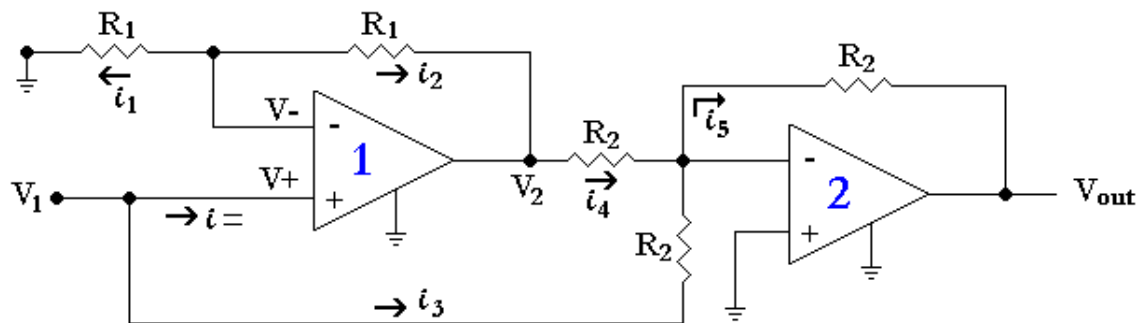

Op Amp #1 :

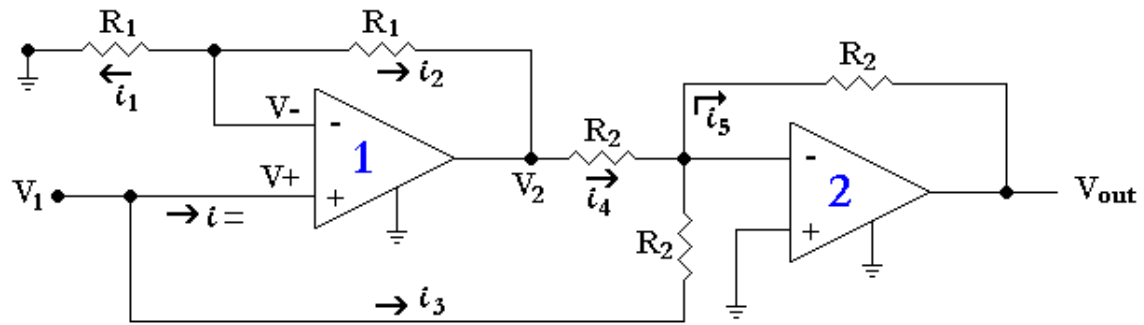

Op Amp #2