




## Enhanced Guided Notes: Set 6

### Parallel Circuits

#### Topics:

- A. Parallel Resistors and Circuits
- B. Power Distribution in a Parallel Circuit
- C. Voltage Sources in Parallel
- D. Open and Short Circuits
- E. Kirchhoff's Current Law
- F. Current Divider Rule
- G. Loading Effects of Instruments
- H. Series-Parallel Circuits

#### A. Parallel Resistors and Circuits

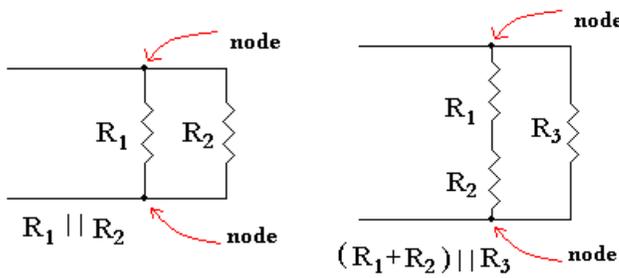


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

Conductance = \_\_\_\_\_

$$\therefore G_T =$$


\* Examples:

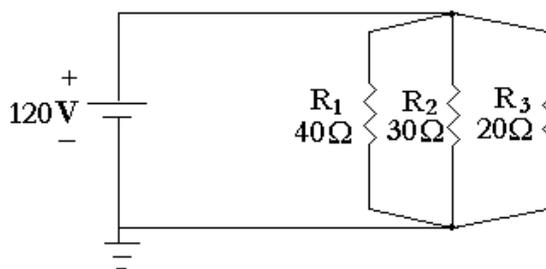

Calculate  $R_{eq}(R_T)$

Are the resistors in parallel?

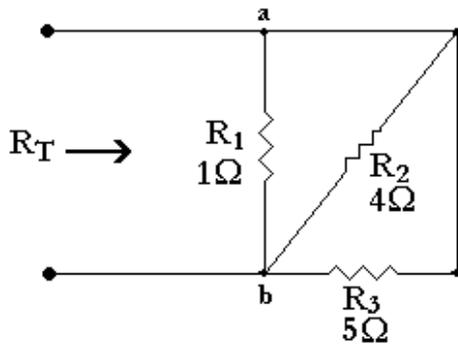Which parallel element has the least conductance?




Calculate  $R_{eq}$  ( $R_T$ )

Are the resistors in parallel?

C

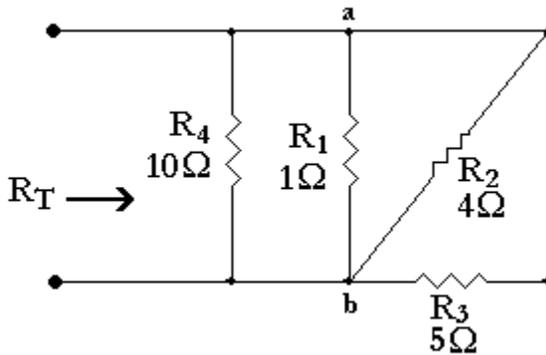Now, what happens if one additional resistor is added to nodes a and b?



$R_T =$


Conclusion:

If all four resistors ( $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ) have the same resistance value (i.e.  $R$ ):

$$R_T = \underline{\hspace{2cm}}$$

SPECIAL CASE: If two resistors are in parallel, then

$$R_T = \underline{\hspace{2cm}}$$

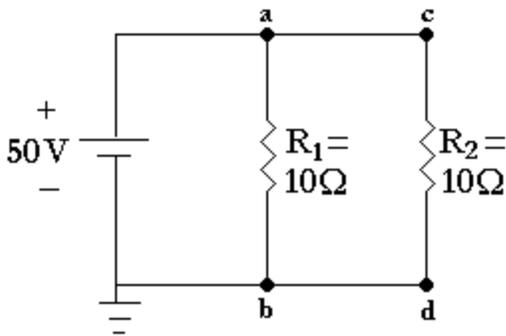

The voltage is always the same across parallel elements.


$$V_{ab} = 50V$$

$$V_{cd} = \quad \quad \quad \text{Why?}$$

$$\therefore V_{ab} = V \quad = V \quad = 50V$$

$$\therefore R_2 = 10 \Omega$$

How do we find  $I_S$ ?

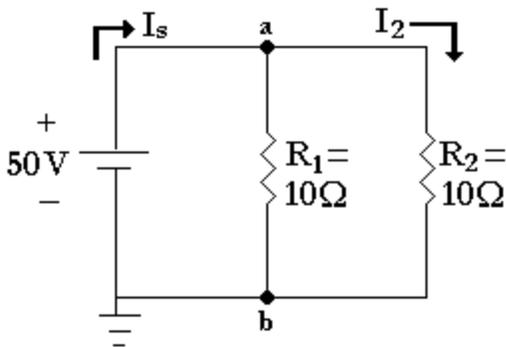

Why?

How do we find  $I_1$  and  $I_2$ ?

We need to use \_\_\_\_\_ law.

We know that  $V_{ab} = V_{R1} = V_{R2} = 50V$

$$\therefore I_1 = \quad =$$


$$I_2 = \quad =$$

From  $I_S$ ,  $I_1$  and  $I_2$ , we can conclude that

$$I_S = \quad =$$


✱ Example:

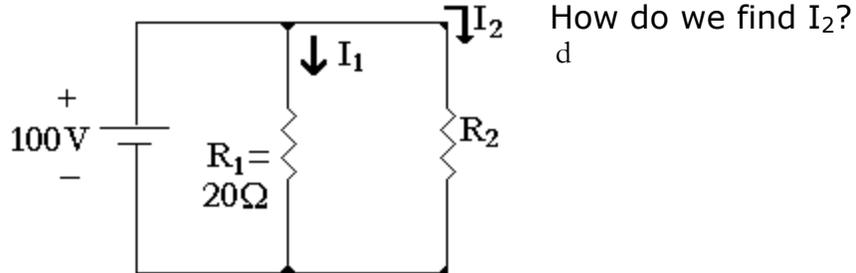Find the current in the  $R_2$  branch of the circuit below. Let's assume  $R_T = 10 \Omega$



✱ Example:

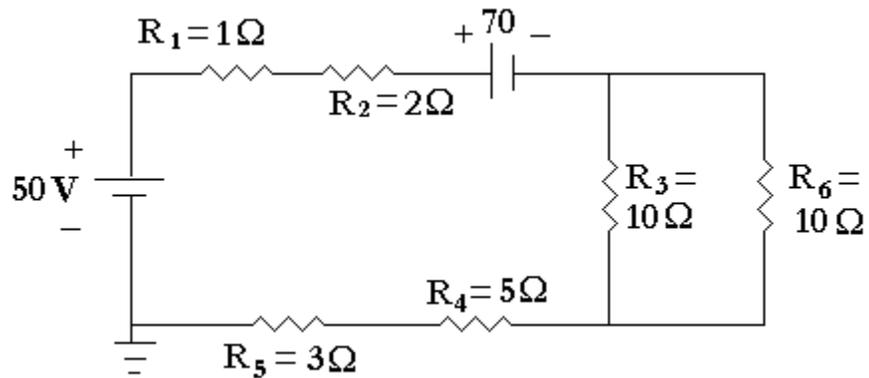What is the voltage across the  $10 \Omega$  resistor in the circuit below?



What is the first step to solve this problem?

$$R_{eq1} = R_3 \parallel R_6 \quad \sim > \quad R_{eq1} = \underline{\hspace{2cm}} = \underline{\hspace{2cm}} \Omega$$


Redraw the circuit

•

•
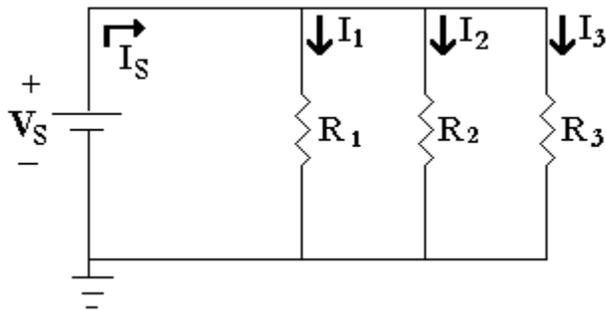
### B. Power Distribution in a Parallel Circuit


Power applied by the voltage source will equal that dissipated by the resistive element.



$$P_S = P_{R1} + P_{R2} + P_{R3}$$

$$V_S I_S = \underline{\hspace{2cm}} + \underline{\hspace{2cm}} + \underline{\hspace{2cm}}$$


### C. Voltage Sources in Parallel

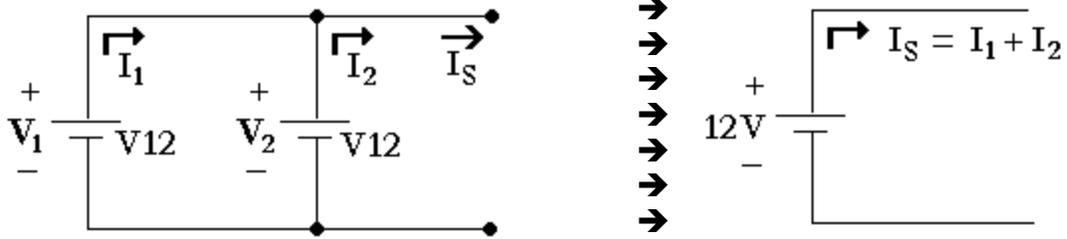

The primary reason for placing two or more batteries or supplies in parallel is to \_\_\_\_\_

What about the total power?

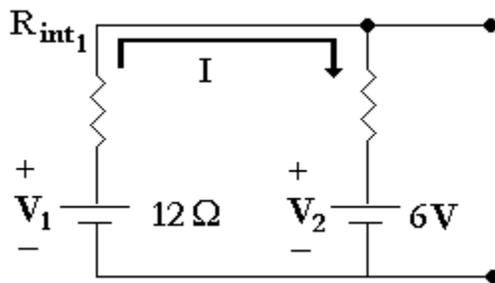What will happen if two batteries of different voltages are placed in parallel?




$$I = \frac{V_1 - V_2}{R_{int1} + R_{int2}}$$

Conclusions:


## D. Open and Short Circuits

What is an open circuit?

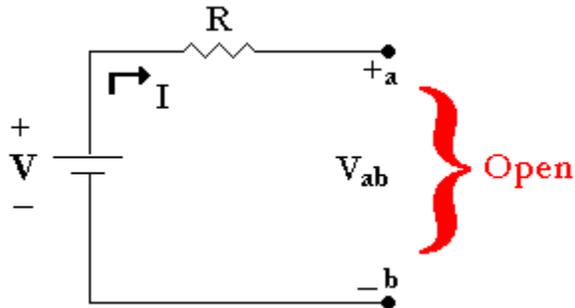


$$I =$$

$$V_{ab} =$$

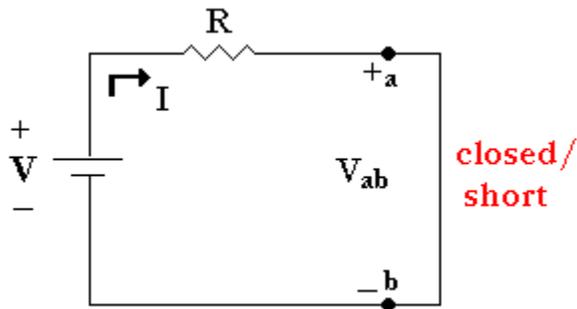

$$I =$$


$$V_{ab} =$$

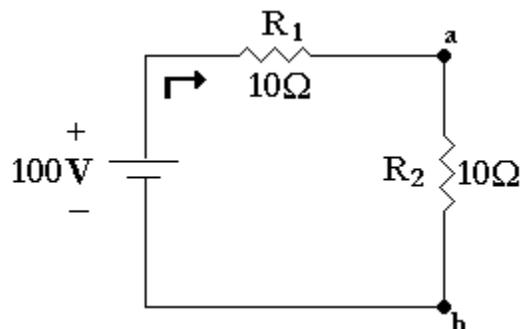
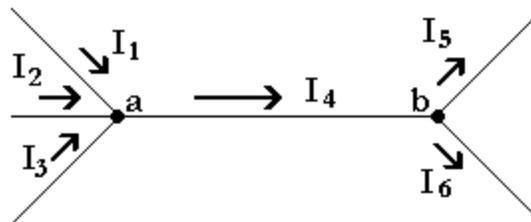
## E. Kirchhoff's Current Law (KCL)


"The algebraic sum of the currents entering and leaving a junction of a network is zero."

$$\therefore \sum I_i + \sum I_o = 0 \quad \rightarrow \quad \sum I_i = \sum I_o$$



$$\sum I_i = \sum I_o$$

\* Example:

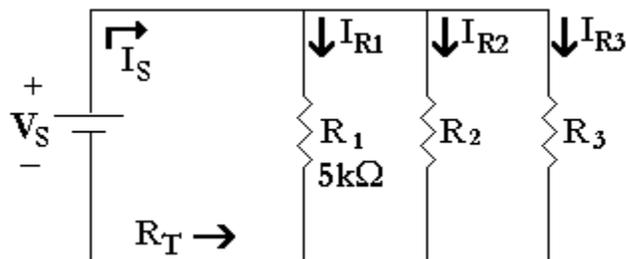

Let's say

$$I_{R1} = 2 \text{ mA}$$

$$I_{R2} = 5 \text{ mA}$$

$$I_{R3} = 10 \text{ mA}$$

Find:

a.  $I_S$


b.  $V$

c.  $R_2$

d.  $R_T$

### F. Current Divider Rule

(From Previous Example)

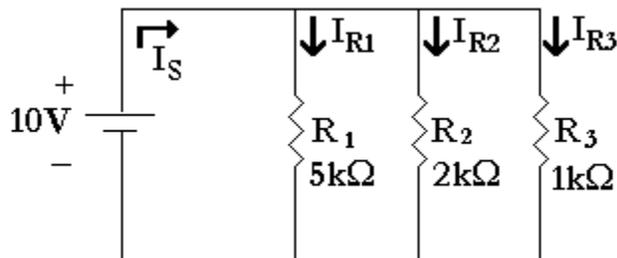

Applying KCL

$$I_S = I_1 + I_2 + I_3$$
$$17\text{mA} = 2\text{mA} + 5\text{mA} + 10\text{mA}$$

$$I_2 = 2.5 I_1$$

$$I_2 = R_1 / R_2 * I_1$$

Similarly,  $I_3 = 5I_1$

$$I_3 = \text{_____} I_1$$

Now, what do we know about the connection between  $I_S$  and  $I_1$ ,  $I_2$ , and  $I_3$ ?

$$I_S = \frac{V}{R_T}$$

Since  $V_1 = V_2 = V_3 = V$

$$\therefore V = I_1 R_1 = I_2 R_2 = I_3 R_3$$

Now, if we substitute  $V$  with  $I_1 R_1$  or  $I_2 R_2$  or  $I_3 R_3$


$$\therefore I_S = \underline{\hspace{2cm}} = \underline{\hspace{2cm}} = \underline{\hspace{2cm}}$$

$$\therefore I_1 =$$

$$\therefore I_2 =$$

$$\therefore I_3 =$$

Special Case: 2-Parallel Resistors

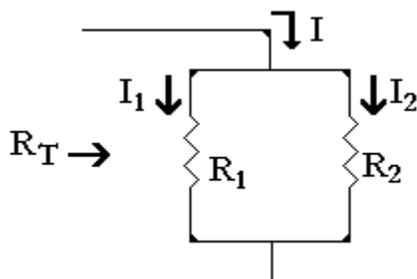

How do we find  $I_1$  and  $I_2$ ?

$$R_T = \underline{\hspace{2cm}}$$

$$I_1 = R_T / R_1 * I = \underline{\hspace{2cm}}$$


$$\therefore I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

Conclusions:

\* Example:

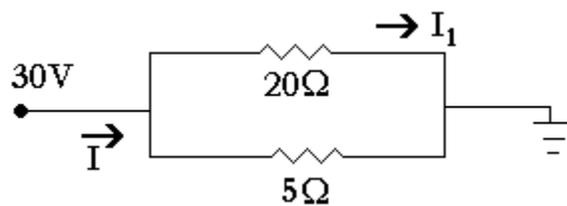
Find the currents  $I_1$  and  $I$  for the following circuit:



How do we solve this problem?

## G. Loading Effects of Instruments

Ammeter

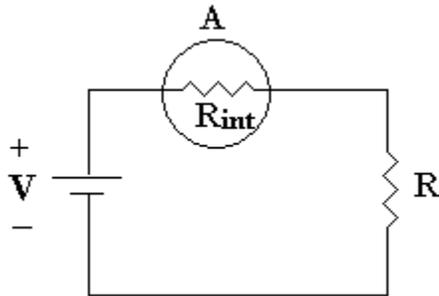


$R_{int}$  is in \_\_\_\_\_ with the branch in which we are measuring the current.

$\therefore$  ideal  $R_{in}$  is \_\_\_\_\_

Why?

Voltmeter

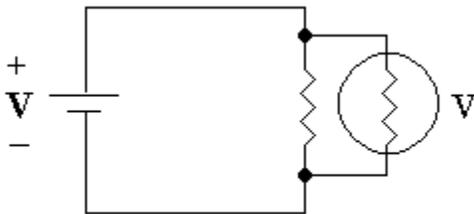

$R_{int}$  is in \_\_\_\_\_ with the branch in which we are measuring the voltage.


$\therefore$  ideal  $R_{in}$  is \_\_\_\_\_

Why?

## H. Series-Parallel Circuits


It is formed by a combination of series and parallel elements

\* Examples:

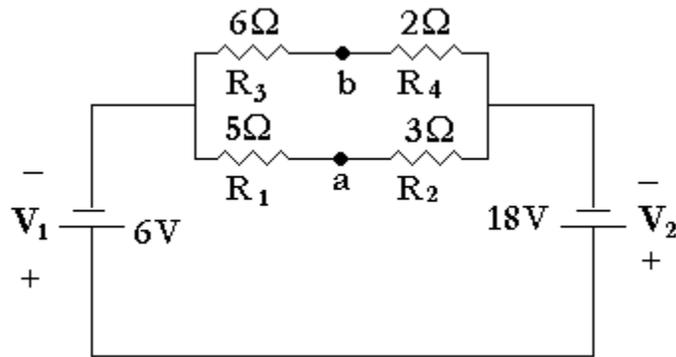

Find:  
 $V_1$   $V_3$   $V_{ab}$  and  $I$

Redraw the circuit

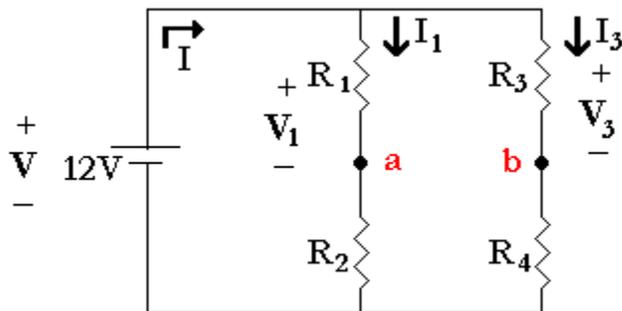

$$V_1 =$$

$$V_3 =$$

$$V_{ab} =$$


Applying Ohm's Law

$$I_1 =$$

$$I_3 =$$

Applying KCL  $\sim > I =$

\* Example:

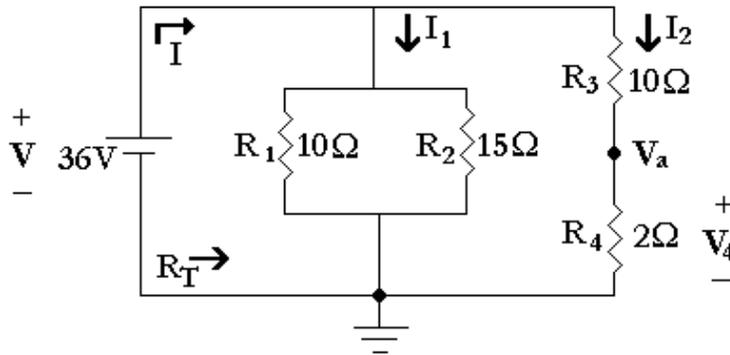

Find:

a.  $R_T$

b.  $I$ ,  $I_1$  and  $I_2$

c.  $V_4$