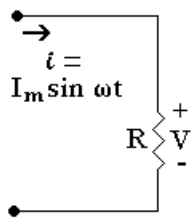


Enhanced Guided Notes: Set 13

Series and Parallel AC Circuits

Resistive Elements



Ohm's Law

$$I_m = V_m/R \quad \text{or} \quad V_m = I_m R$$


$$\star \quad R = 5 \Omega \quad \sim > \quad Z_R =$$

$$V = 100 \sin \omega t \quad \sim > \quad V_m =$$


$$\therefore V =$$

$$I = V/Z_R = \underline{\hspace{2cm}} =$$

$$\therefore i =$$

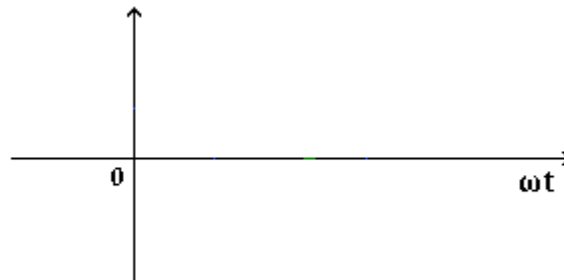

Inductive Reactance

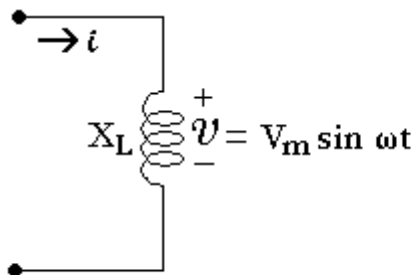

$$I = \frac{V \angle 0^\circ}{X_L \angle \theta_L} = \frac{V}{X_L} \angle 0^\circ - \theta_L$$

$$i = \sqrt{2} \left(\frac{V}{X_L} \right) \sin (\omega t - 90^\circ)$$

$$Z_L = X_L \angle 90^\circ$$

Why does Z_L have a $+ 90^\circ$ phase angle?

★ $X_L = 3\Omega$ $\sim \angle Z_L =$

$V = 24 \sin \omega t$ $\sim \angle V_m =$

$V =$


$I = \frac{V}{Z_L} =$

$=$

$\therefore i =$



Capacitive Reactance

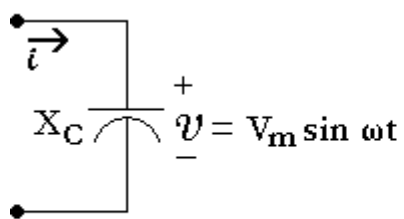

$$I = \frac{V \angle 0^\circ}{X_C \angle \theta_C} = \frac{V}{X_C} \angle 0^\circ - \theta_C$$

$$i = \sqrt{2} \left(\frac{V}{X_C} \right) \sin (\omega t - 90^\circ)$$

$$Z_C = X_C \angle -90^\circ$$

Why does Z_C have a -90° phase angle?

$$\star \quad X_C = 2\Omega \quad \leadsto Z_C =$$


$$V = 15 \sin \Omega t \leadsto V_m =$$

$$V =$$


$$I = V/Z_C = \underline{\hspace{2cm}}$$

$$\therefore I =$$

$$i =$$

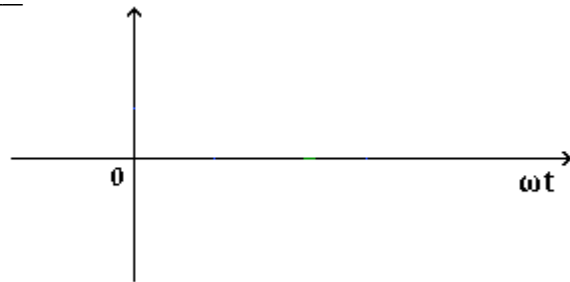

Series

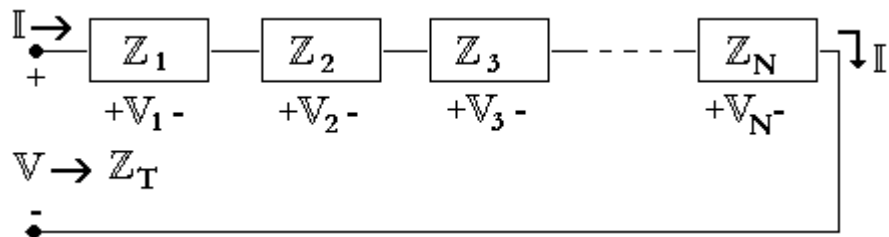

$$Z_T =$$


$$I = \underline{\hspace{2cm}} \text{ or } \underline{\hspace{2cm}}$$

$$V_1 =$$

$$V_2 =$$

$$V_N =$$

Parallel

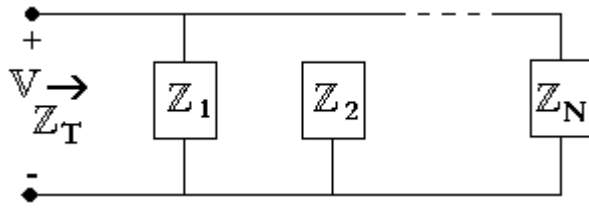

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$


Terms: susceptance (B)

Admittance (Y)

Unit:

R-L-C Circuits

★

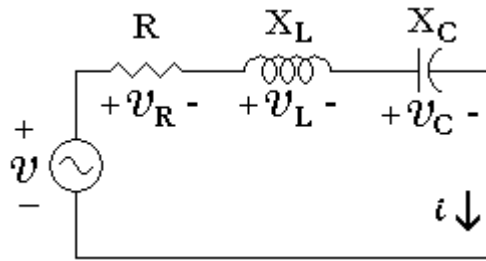

Let $R = 2\Omega$
 $X_L = 7\Omega$
 $X_C = 3\Omega$

Redraw the circuit

Phasor notation

$$\mathbf{V} =$$

$$\mathbf{Z}_T =$$

$$\mathbf{I} = \mathbf{V} / \mathbf{Z}_T$$

$$\mathbf{V}_R =$$

$$\mathbf{V}_L =$$

$$\mathbf{V}_C =$$

$$\therefore i =$$

$$V_R =$$

$$V_L =$$

$$V_C =$$

$$P_T = P_R + P_L + P_C$$


$$= V_R I \cos \phi_R + V_L I \cos \phi_L + V_C I \cos \phi_C$$

$$=$$

$$\text{Power factor} \rightarrow \text{pf} = \cos \phi_T$$

$$=$$


$$=$$

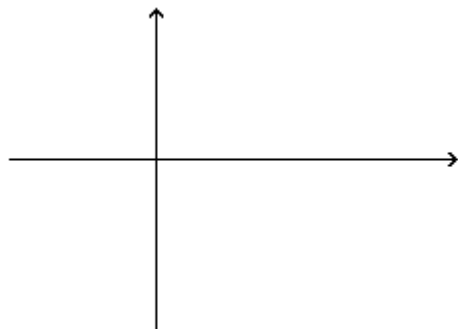

Another way to find V_R , V_L , V_C , P_T


How?

★

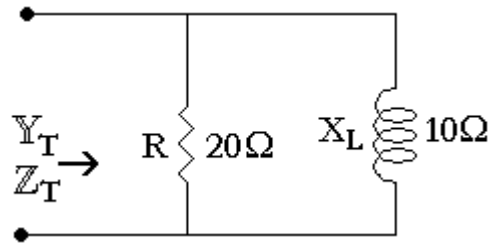



a. Input impedance

b. The impedance diagram

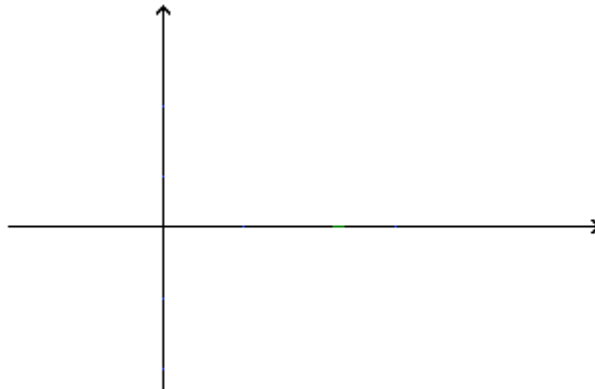


c. The admittance of each parallel branch

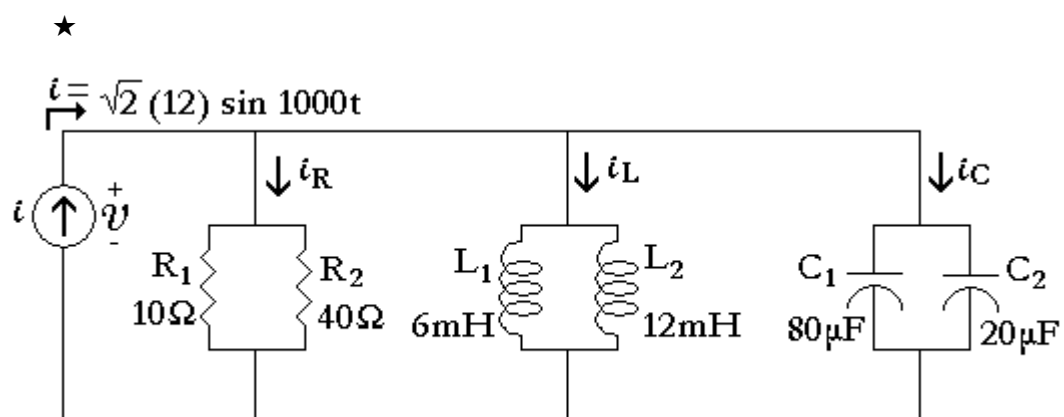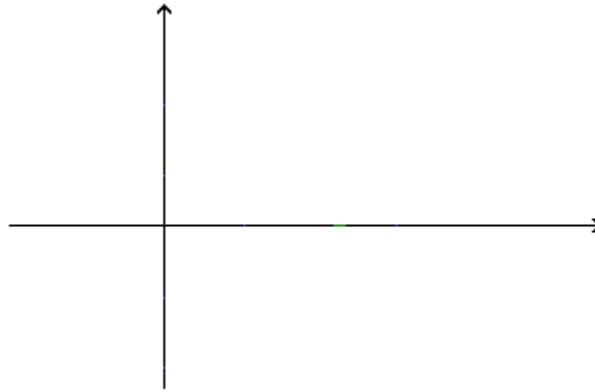d. The input admittance and admittance diagram



a. Find Y_T and Z_T

b. Sketch the admittance diagram

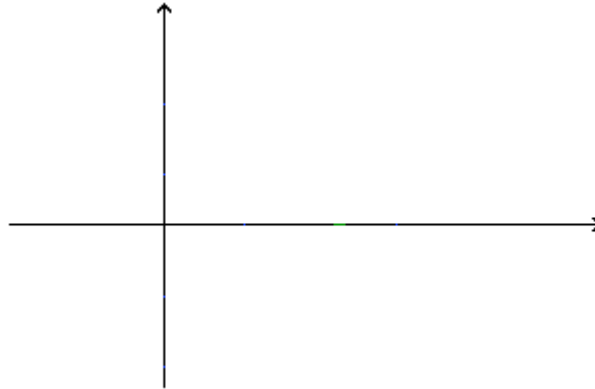

c. Find V and I_L

$$V =$$

$$I_L =$$

- d. Compute the power factor of the network and the power delivered to the network.

$$\text{pf} =$$

$$P =$$

- e. The equivalent circuit