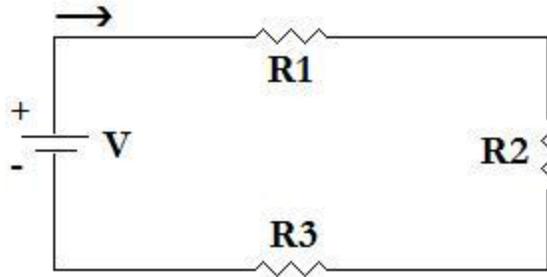


Voltage and Current

Topics:

- A. Series Resistors/Circuits
- B. Power Distribution in a Series Circuit
- C. Voltage Sources in a Series Circuit
- D. Kirchhoff's Voltage Law
- E. Voltage Division in a Series Circuit
- F. Voltage Regulation and the Internal Resistance of Voltage Sources

A. Series Resistors / Circuits




$$I_{R1} = I_{R2} = I_{R3} =$$

$$I = \underline{\hspace{2cm}}$$

$$R_{TOTAL} = R_1 +$$

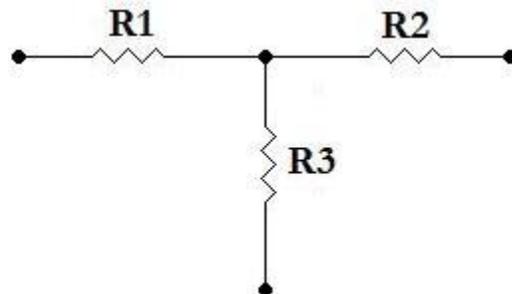In general, $R_T = R_1 + R_2 + R_3 + \dots + R_N$



Are these resistors in series?

✳ Examples:


Discovered by Georg Simon Ohm

$\Delta T = 0 \rightarrow$ Double V \rightarrow Double I
Triple V \rightarrow Triple I



Conclusions

-
-



Now, we can say that $\frac{V}{I} = R$

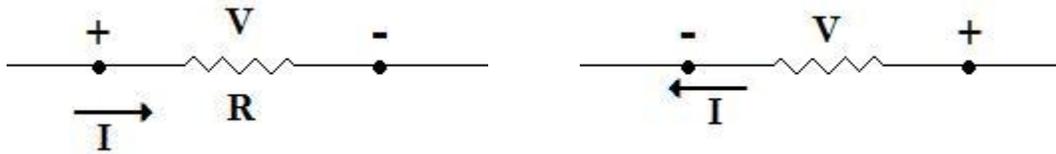

* Examples:

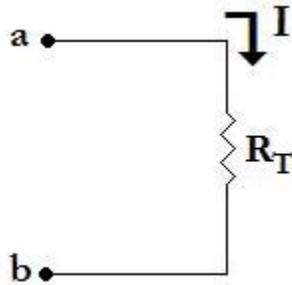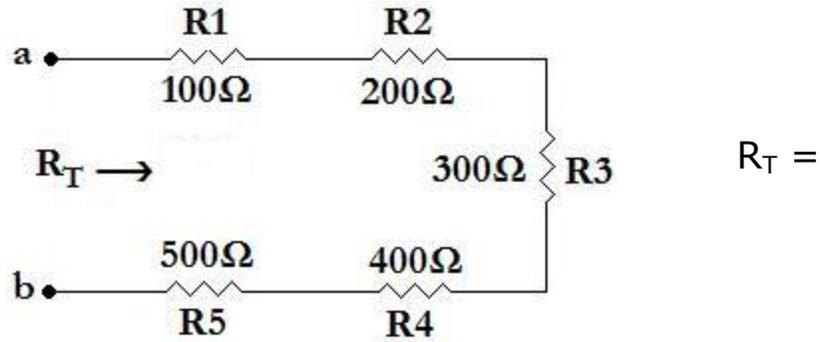


If $V_{ab} = 15V$ then $I =$

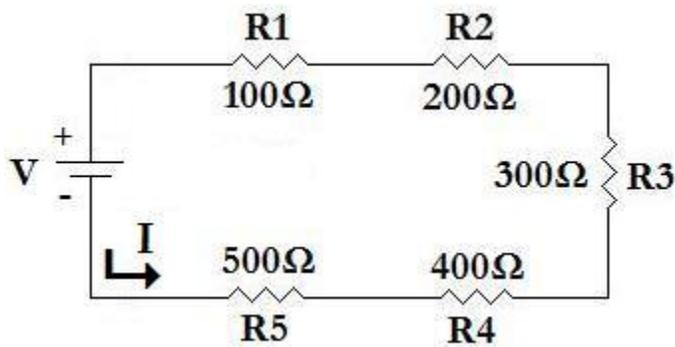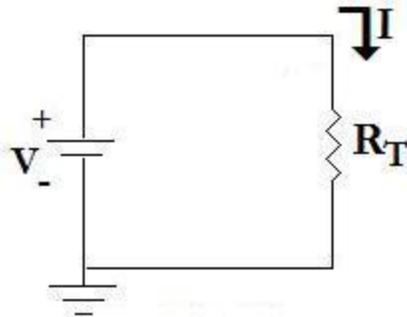

If $V=15$

$I =$

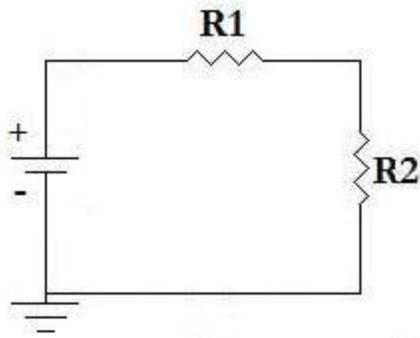A $20\text{k}\ \Omega$ resistor and a $15\text{k}\ \Omega$ resistor are connected in series to a 140 V source. Find the voltage drop across the $15\text{k}\ \Omega$ resistor.



How do we solve this problem?


Why?

Conclusions?

B. Power Distribution in a Series Circuit

$$P_{\text{applied}} = P_{\text{dissipated (absorbed)}}$$

Let's consider this situation

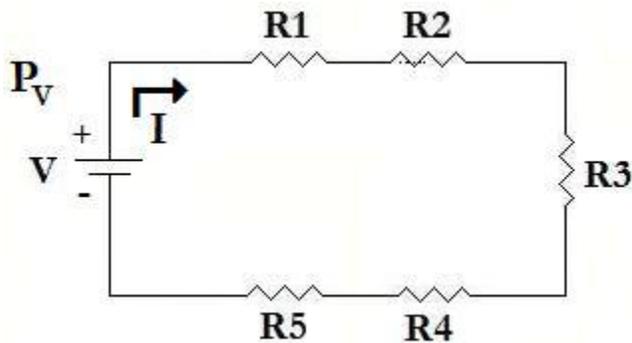

$$P_V = P_{R1} + P_{R2} + P_{R3} + P_{R4} + P_{R5}$$

Let $V = 15 \text{ V}$

$R1 = 100\Omega$, $R2 = 200\Omega$, $R3 = 300\Omega$, $R4 = 400\Omega$ and
 $R5 = 500\Omega$


a. $R_T =$

b. $I =$

c. $P_V =$


d. How do you calculate P_{R1} , P_{R2} , P_{R3} , P_{R4} , and P_{R5} ?

C. Voltage Sources in a Series Circuit

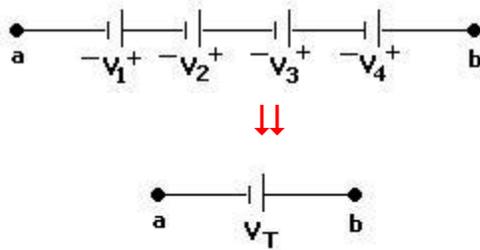

$$V_T =$$

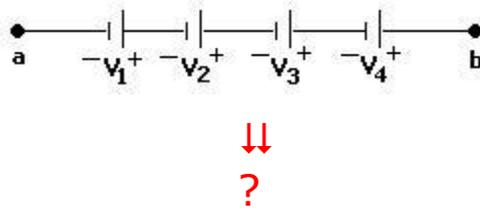Now, what happens if we have the following arrangement of voltage sources?



Conclusions

- V
- I
- P

D. Kirchhoff's Voltage Law


Kirchhoff's Voltage Law (KVL) was developed by Gustav Kirchhoff in the mid 1800s.

KVL requires _____


"The algebraic sum of the potential rises or drops around a closed loop is zero."

$$\therefore \sum_{\text{loop}} V = 0 \quad \rightarrow \quad \sum_{\text{loop}} V_{\text{Rises}} =$$

* Examples:

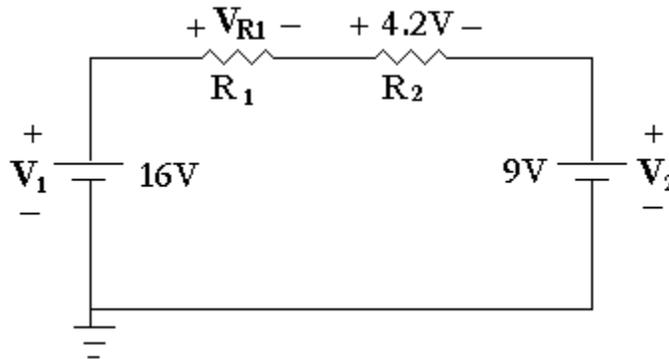

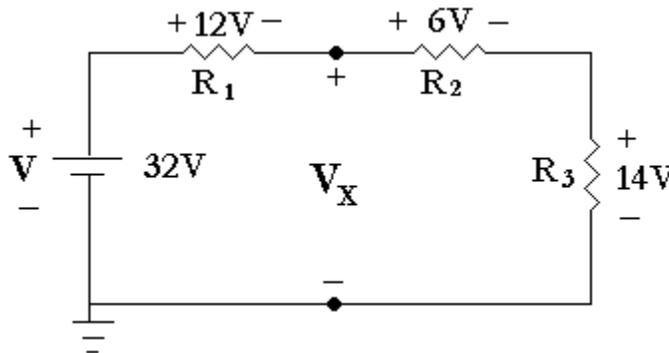Use Kirchhoff's Vol. Law to determine V_{R1}




Use KVL to determine V_X

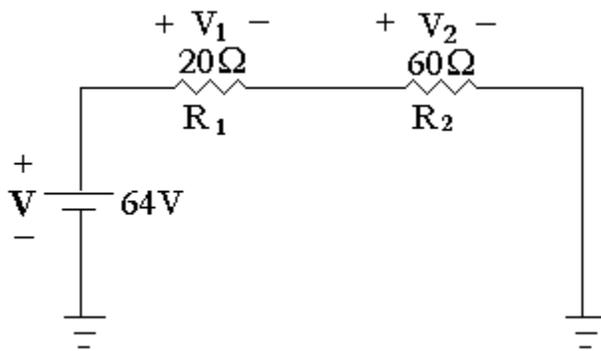E. Voltage Division in a Series Circuit

From KVL, we know that $\therefore \sum V = 0$

How will a resistor's value affect the voltage across the resistor?




a. What can we say about the voltage across R_2 compared to that across R_1 ?

b. $V_1 =$


c. $V_2 =$

* Example:

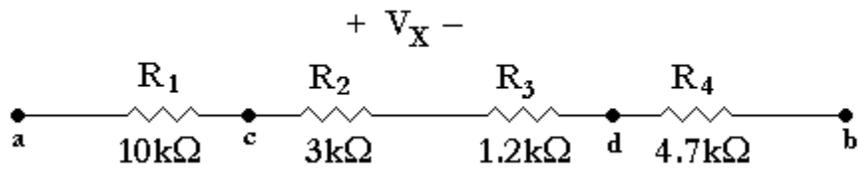


$V_{cd} = 5.6 \text{ V}$
Find V_x

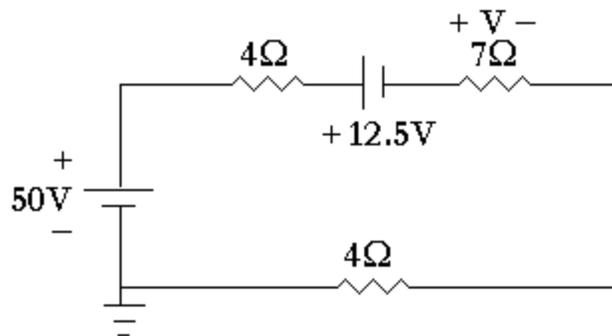Find I and the voltage across the 7Ω resistor for the following network.




How do we solve this problem? Why?

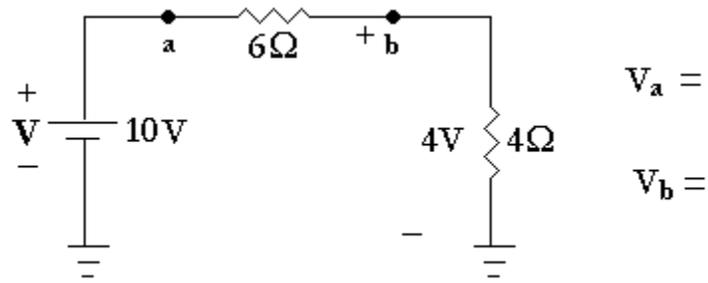
What is the difference between V_a and V_{ab} ?



$$V_{ab} = V_a - V_b$$

|

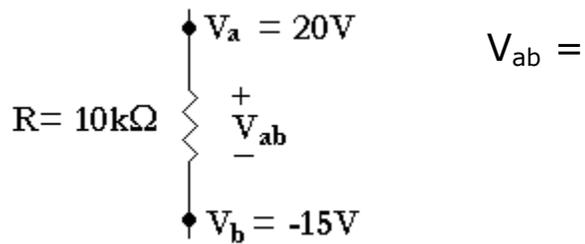

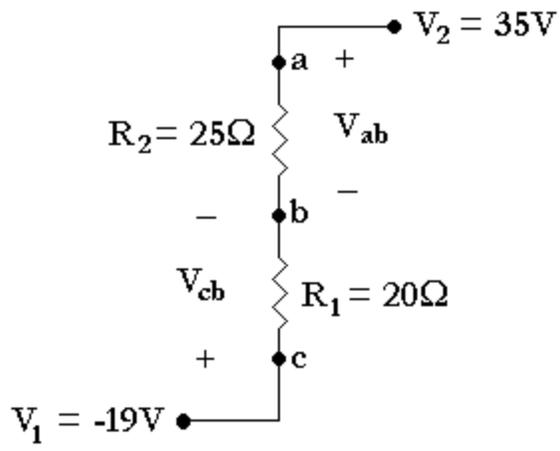

Find V_{ab} , V_{cb} and V_c

How do we approach this problem?

Redraw






- $I =$

$V_{ab} =$

$V_{cb} =$

$V_c =$

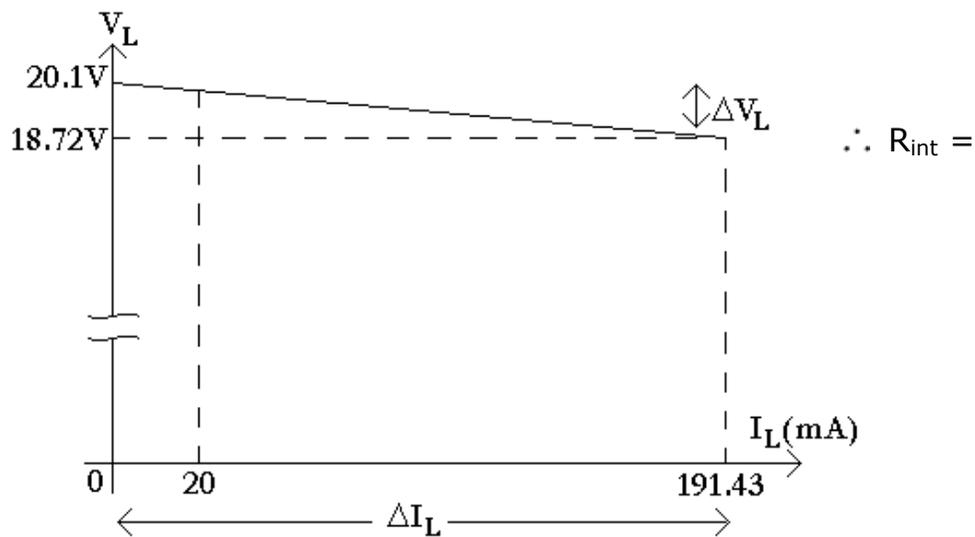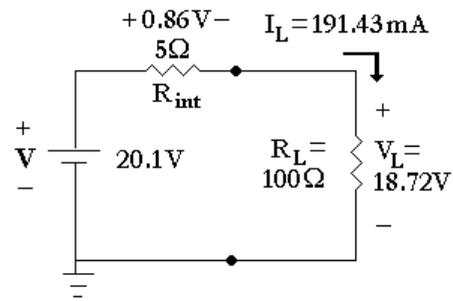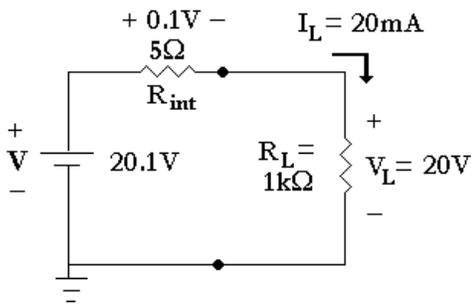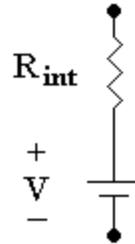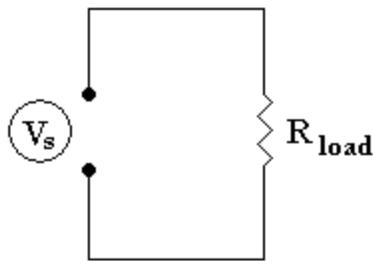F. Voltage Regulation and the Internal Resistance of Voltage Source



Voltage Regulation (VR) = Load Regulation

$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} * 100\%$$

Conclusions: