

## Enhanced Guided Notes: Set 8

### Voltage and Current

#### Topics:

- A. Superposition Theorem
- B. Thevenin's Theorem
- C. Norton's Theorem
- D. Maximum Power Transfer Theorem

#### A. Superposition Theorems

Purposes:

- Analyze networks that have two or more sources
- Determine the impact of a particular source on the response of the entire system


"The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source."

How?


- Voltage source  $\sim >$




- Current source  $\sim >$

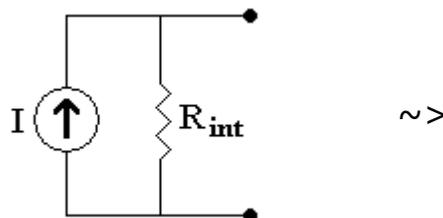


\* Examples:

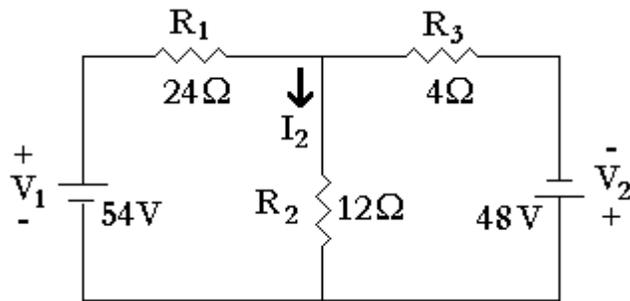


Find:  $I_2$

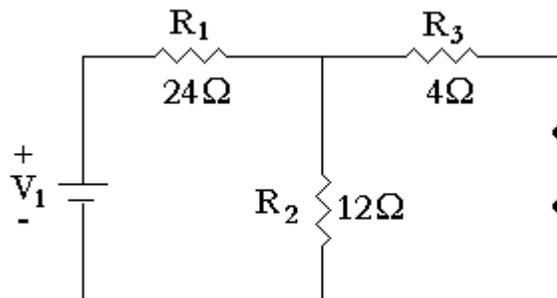

What do we need to do next?


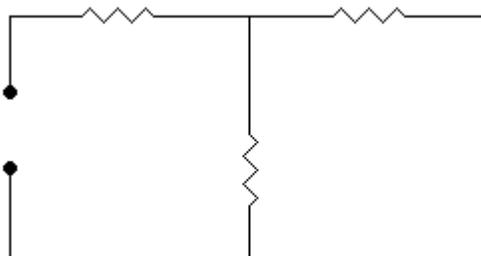


What do we need to do next?

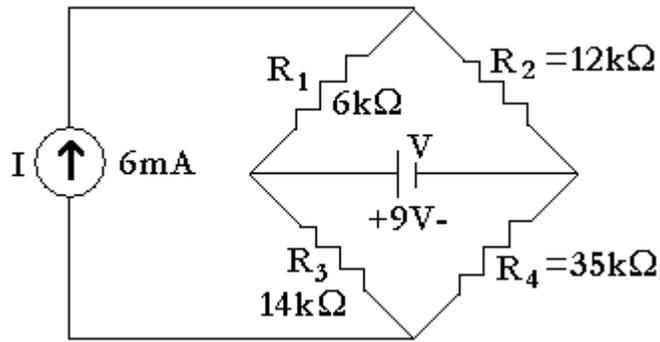

Find  $I_2$

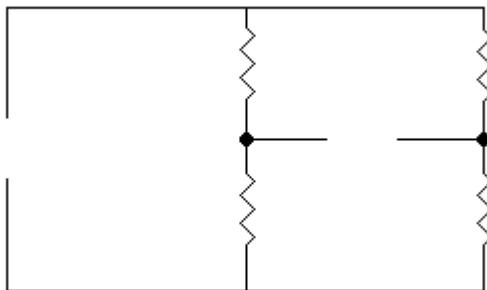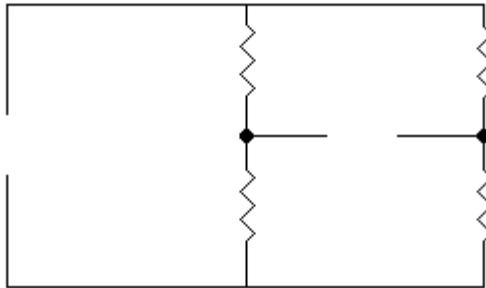
What is our strategy to solve this problem?



## B. Thevenin's Theorem


Purposes:

\* Examples:

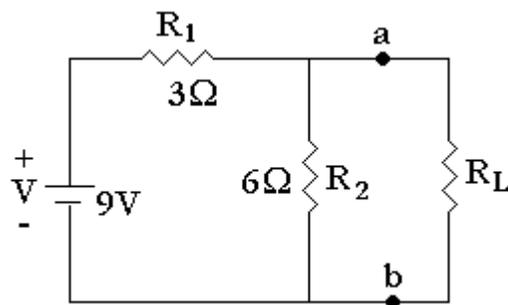

Find the Thevenin equivalent circuit for the network.

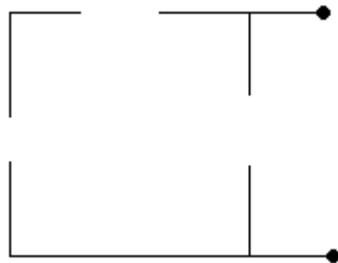
Step 1: Remove the load and mark the terminals of the two-terminal network



Step 2: Calculate  $R_{Th}$


$$R_{Th} =$$

Step 3: Calculate  $V_{Th}$

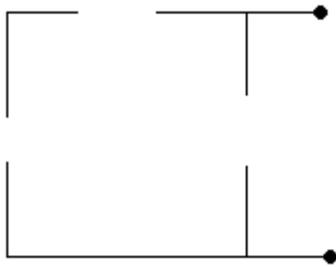

$V_{Th} =$

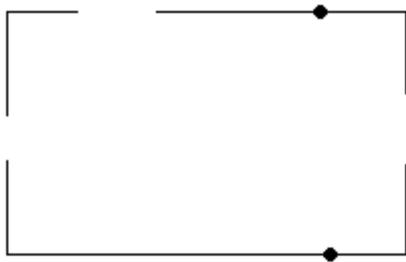Step 4: Draw the Thevenin equivalent circuit



If  $R_L = 1\Omega \sim > I_L =$

$P =$

If  $R_L = 2\Omega \sim > I_L =$


$P =$

If  $R_L = 10\Omega \sim > I_L =$


$P =$


If  $R_L = 100\Omega \sim > I_L =$

$P =$




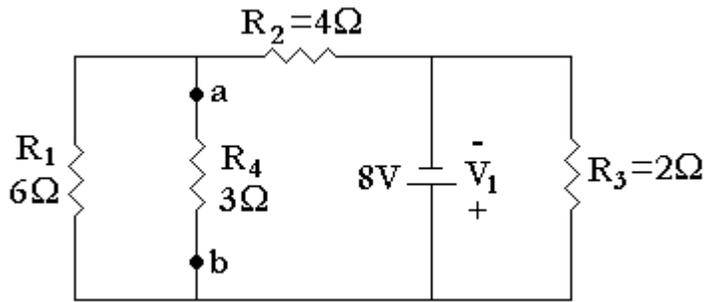



How do we solve this problem?

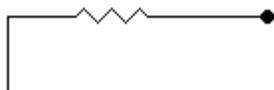

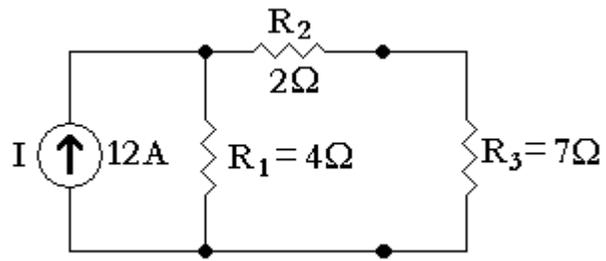


Find the Thevenin equivalent circuit.

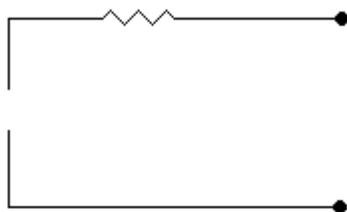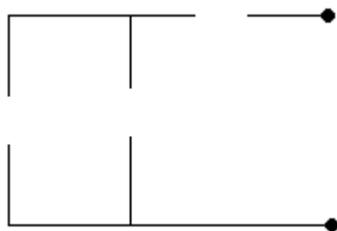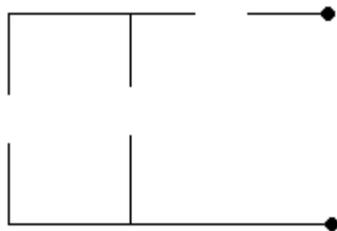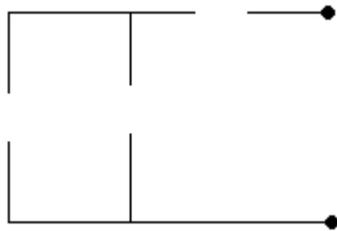


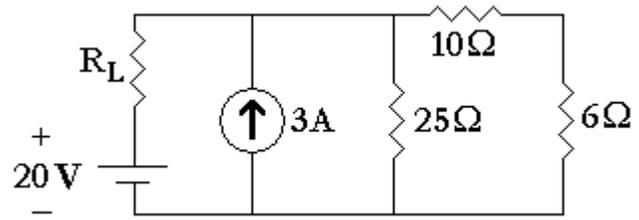

Find the Thevenin equivalent circuit.

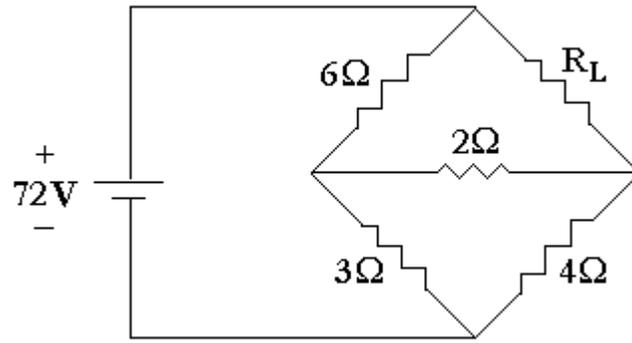


### C. Norton's Theorem

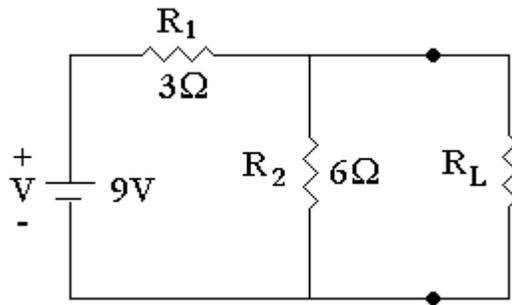


Find the Norton equivalent circuit for the network.

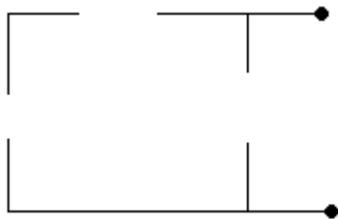Step 1: Remove the  $R_L$  and mark the terminals of the two-terminal network.




Step 2: Calculate  $R_N$

$R_N =$

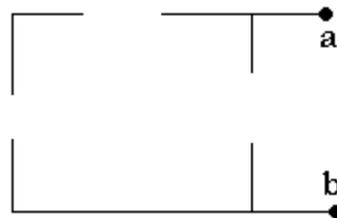


Step 3: Calculate  $I_N$





$I_N =$

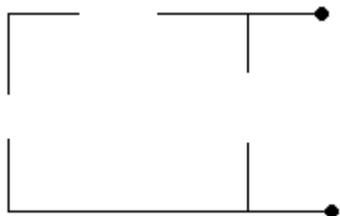


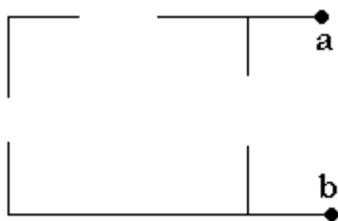Step 4: Draw the Norton equivalent circuit




\* Examples:

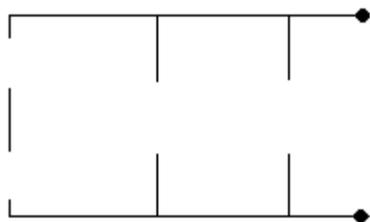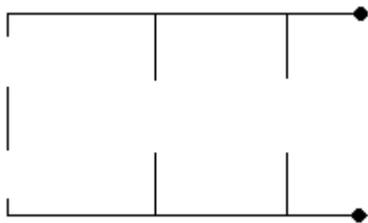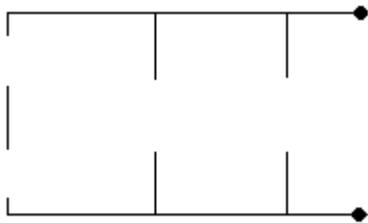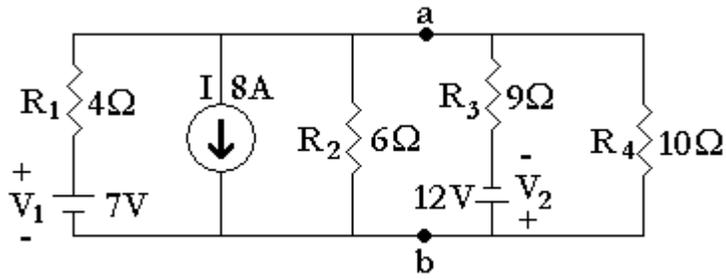

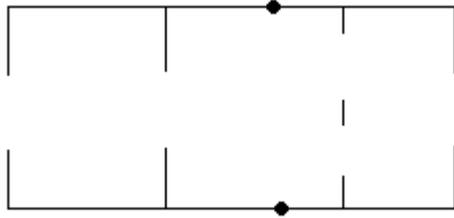


Find the Norton eq. circuit

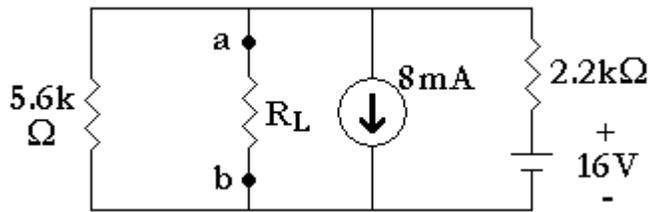

----- □ a

----- □ b

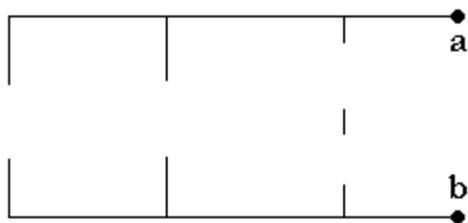

-----□ a

-----□ b


-----□  
a

-----□  
b

## D. Maximum Power Transfer Theorem

A load will receive maximum power from a network when

$$\therefore R_L = R$$

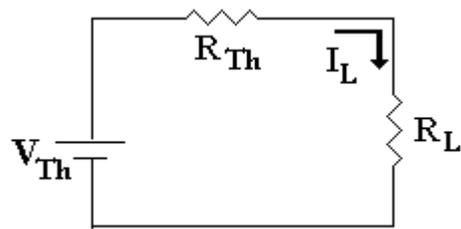

$$I_L =$$

$$P_L =$$

$$\therefore P_{L \text{ max}} =$$